



中国科学院大学  
University of Chinese Academy of Sciences

B0911006Y-01

2024-2025学年春季学期

# 计算机组成原理

Principles of Computer Organization


## 单周期处理器 I

基本组件，如何设计、组装数据通路


主讲教师：石 侃  
shikan@ict.ac.cn

2025年4月9日


# 回顾：冯诺依曼计算机五大部件

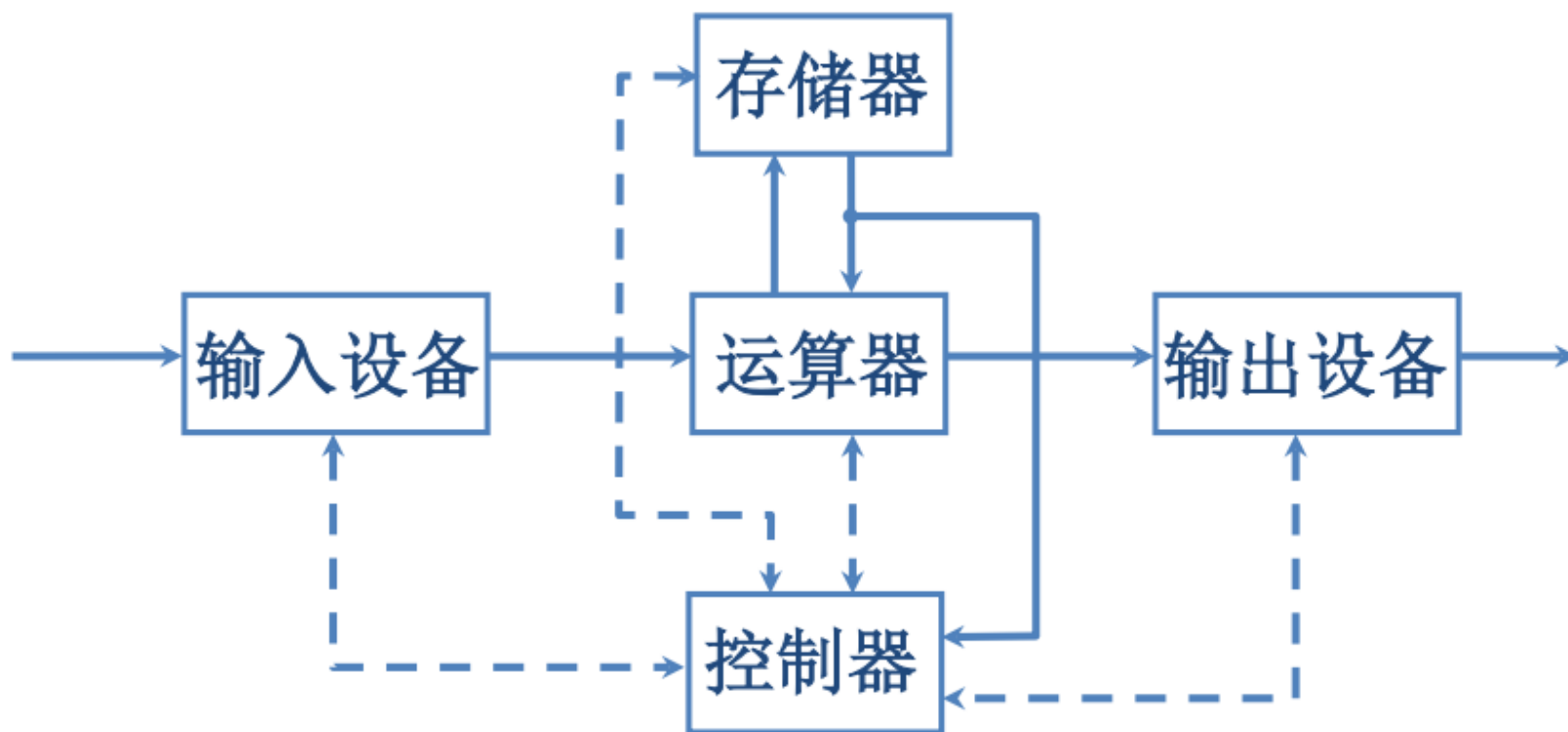

# 回顾：冯诺依曼计算机五大部件

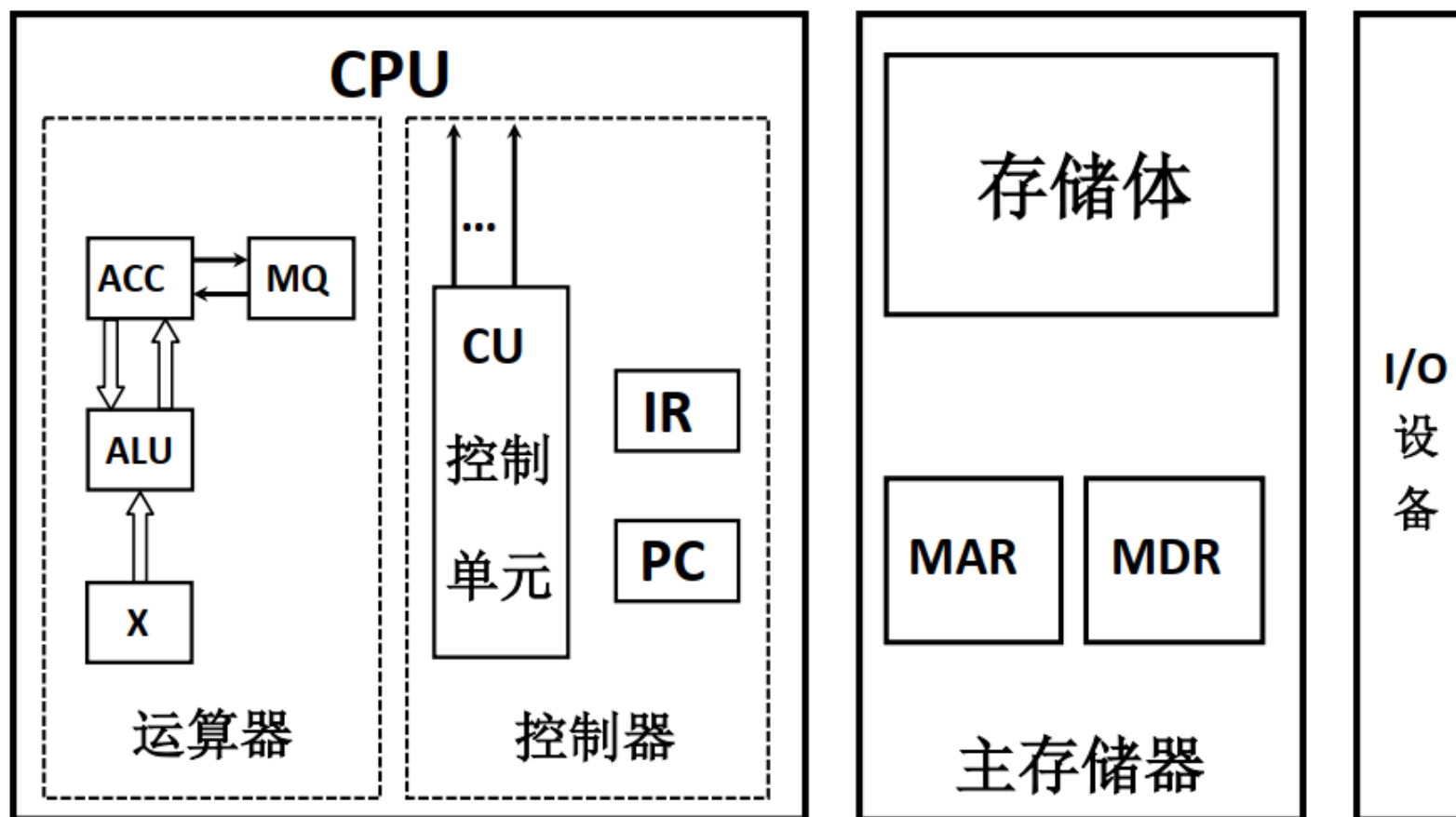

# 回顾：冯诺依曼计算机五大部件

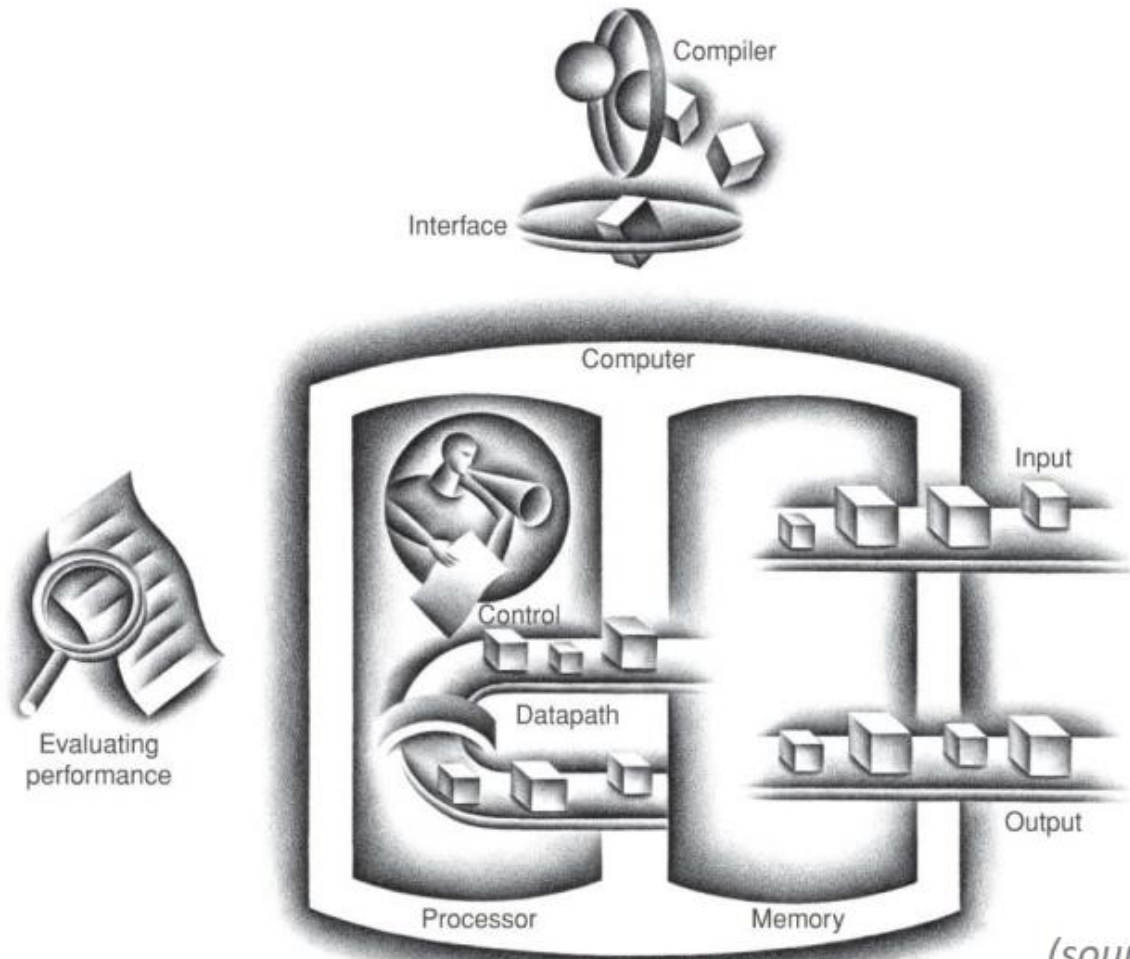

(source: P&H-COD)

# The Processor

- **Processor (CPU):** Implements the instructions of the Instruction Set Architecture (ISA)

# The Processor

- **Processor (CPU):** Implements the instructions of the Instruction Set Architecture (ISA)
  - *Datapath*: part of the processor that contains the hardware necessary to perform operations required by the processor (“the brawn”)
    - 指令执行过程中，数据所经过的路径，包括路径中的部件
    - 是指令执行的部件
    - 组合元件和存储元件通过总线或分散方式连接而成的进行数据存储、处理和传送的路径。

# The Processor


- **Processor (CPU):** Implements the instructions of the Instruction Set Architecture (ISA)
  - *Datapath*: part of the processor that contains the hardware necessary to perform operations required by the processor (“the brawn”)
    - 指令执行过程中，数据所经过的路径，包括路径中的部件
    - 是指令执行的部件
    - 组合元件和存储元件通过总线或分散方式连接而成的进行数据存储、处理和传送的路径。
  - *Control*: part of the processor (also in hardware) which tells the datapath what needs to be done (“the brain”)
    - 对指令进行译码，生成指令对应的控制信号，控制数据通路的动作
    - 是指令的控制部件，对执行部件发出控制信号

# Processor Design Process

- Five steps to design a processor:

- Datapath**
- 1. Analyze instruction set → datapath requirements
  - 2. Select set of datapath components & establish clock methodology
  - 3. Assemble datapath meeting the requirements

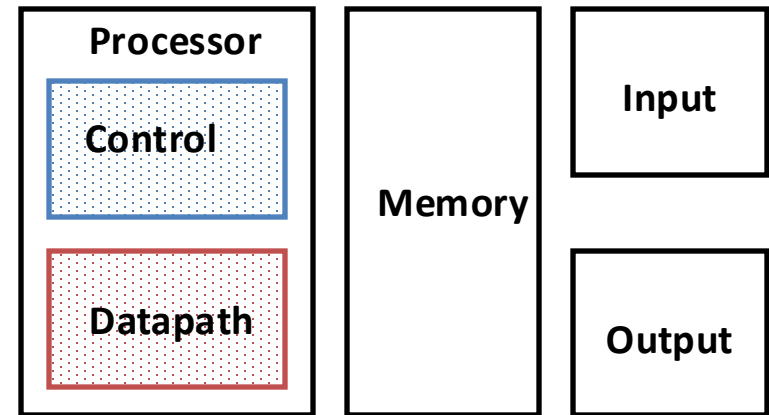
- Control**
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer
  - 5. Assemble the control logic
    - Formulate Logic Equations
    - Design Circuits




 
# The Big Picture: The Performance Perspective

- Processor design (datapath and control) will determine:
  - Clock cycle time
  - Clock cycles per instruction
- Starting today:
  - Single cycle processor:
    - Advantage: One clock cycle per instruction
    - Disadvantage: long cycle time
- $\text{CPUTime(ET)} = \text{IC} \times \text{CPI} \times \text{Cycle Time}$ 
  - 指令数目由编译器和ISA决定
  - 时钟周期和CPU由CPU的设计和实现决定




# Processor Datapath and Control

- We're ready to look at an implementation of a simplified MIPS CPU contains only:
  - memory-reference instructions: `lw, sw`
  - arithmetic-logical instructions: `add, sub, and, or, slt`
  - control flow instructions: `beq`
- Generic Implementation:
  - use the `program counter (PC)` to supply instruction address
  - get the `instruction` from memory
  - read registers
  - use the instruction to decide exactly what to do
- Which instructions will use the ALU after register reading?
  - memory-reference? arithmetic? control flow?
  - **ALL of THESE**
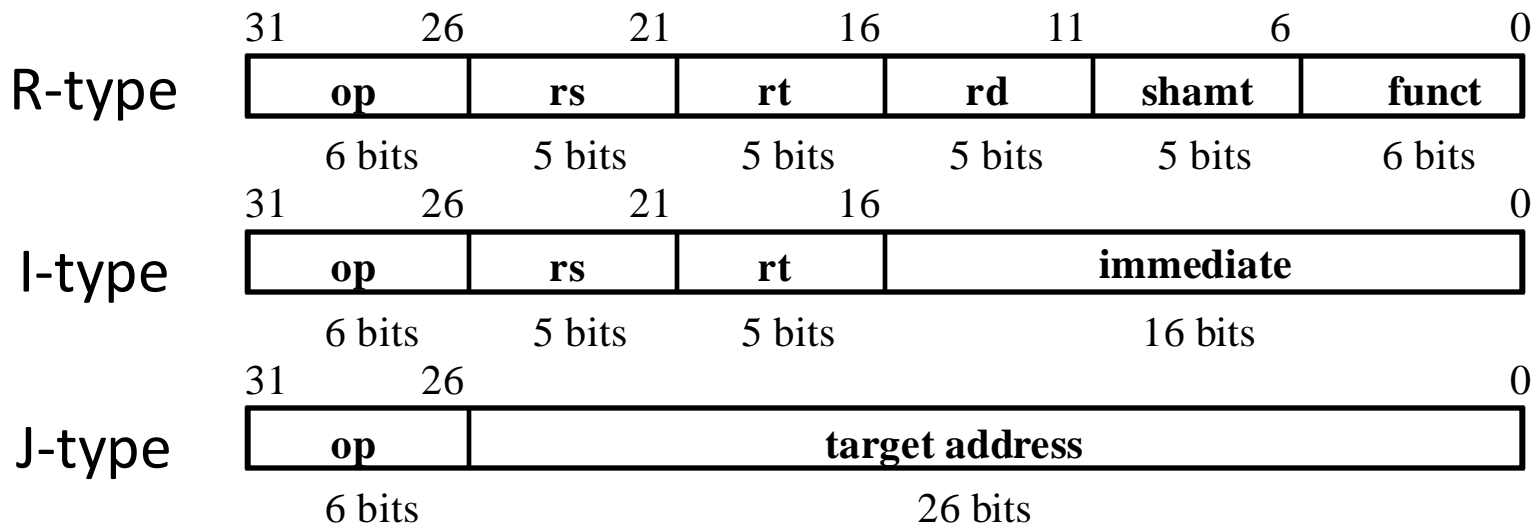
# MIPS Instruction Formats


- 无内部互锁流水级的微处理器  
(Microprocessor without Interlocked Piped Stages)
- All instructions 32-bits long
- 3 Formats:


 
# The MIPS Subset


- R-Type

- `add` rd, rs, rt
- `sub`, `and`, `or`, `slt`




- LOAD and STORE

 - `lw` rt, rs, imm16
- `sw` rt, rs, imm16



- BRANCH:

- `beq` rs, rt, imm16

 

# Basic Steps of Execution

- Instruction Fetch
  - Where is the instruction?

**Instruction memory  
address: PC**
- Decode
  - What's the incoming instruction?
  - Where are the operands in an instruction?

**Register file**
- Execution: ALU
  - What is the function that ALU should perform?

**ALU**
- Memory access
  - Where is my data?

**Data memory  
address: effective address**
- Write back results to registers
  - Where to write?


**Register file**
- Determine the next PC
  -

**Program counter**



# Generic Mechanism of Processor

- Use **Program Counter (PC)** to supply an instruction address
- Get the **instruction** from memory
- Use the instruction to **decide (control)** exactly which **register(s)** to read or write
- Use the instruction to **decide (control)** exactly what **operation(s)** to execute

# Where We're Going: The High-level View

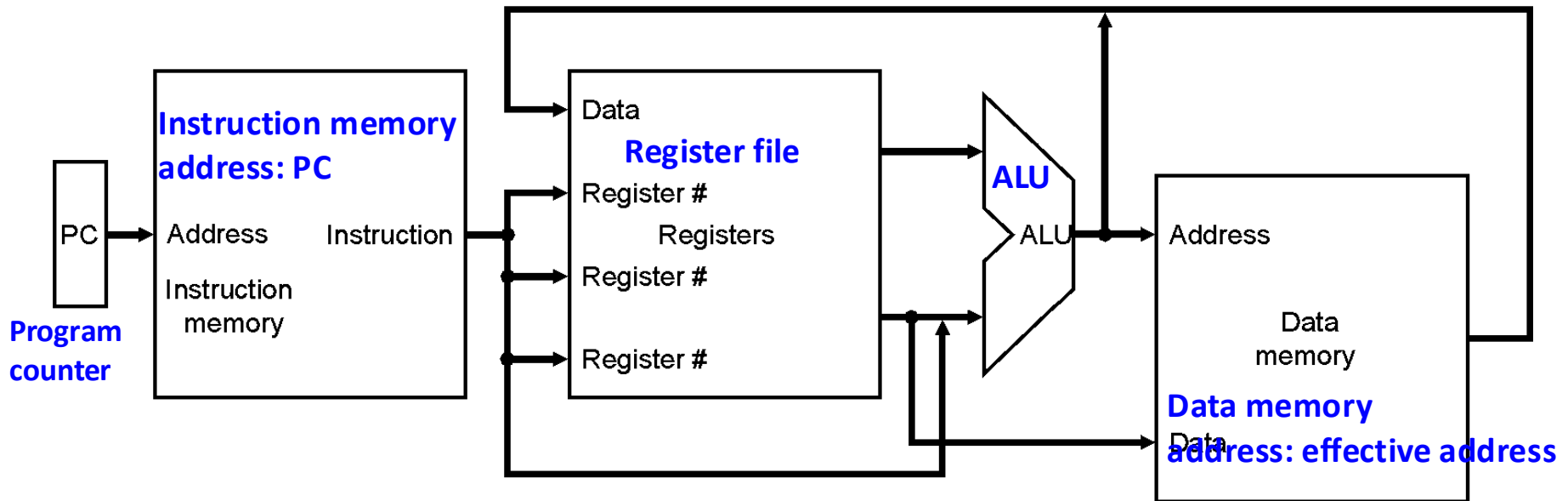

# Review: Two Logical Components

  




# Combinational Elements


- AND-gate

- $Y = A \& B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 


- Adder

- $Y = A + B$

 


- Arithmetic/Logic Unit


- $Y = F(A, B)$

 

# Clocking Methodology (定时方法)

 

 
- **Setup Time:** how long the input must be stable before the CLK trigger for proper input read
- **Hold Time:** how long the input must be stable after the CLK trigger for proper input read
- **CLK-to-Q Delay (锁存延迟) :** how long it takes the output to change, measured from the CLK trigger



- The critical path is the longest delay between any two registers in a circuit
- **Critical path** determines length of clock period
  - The clock period must be longer than this critical path, or the signal will not propagate properly to that next register
  - This includes CLK-to-Q delay and setup delay

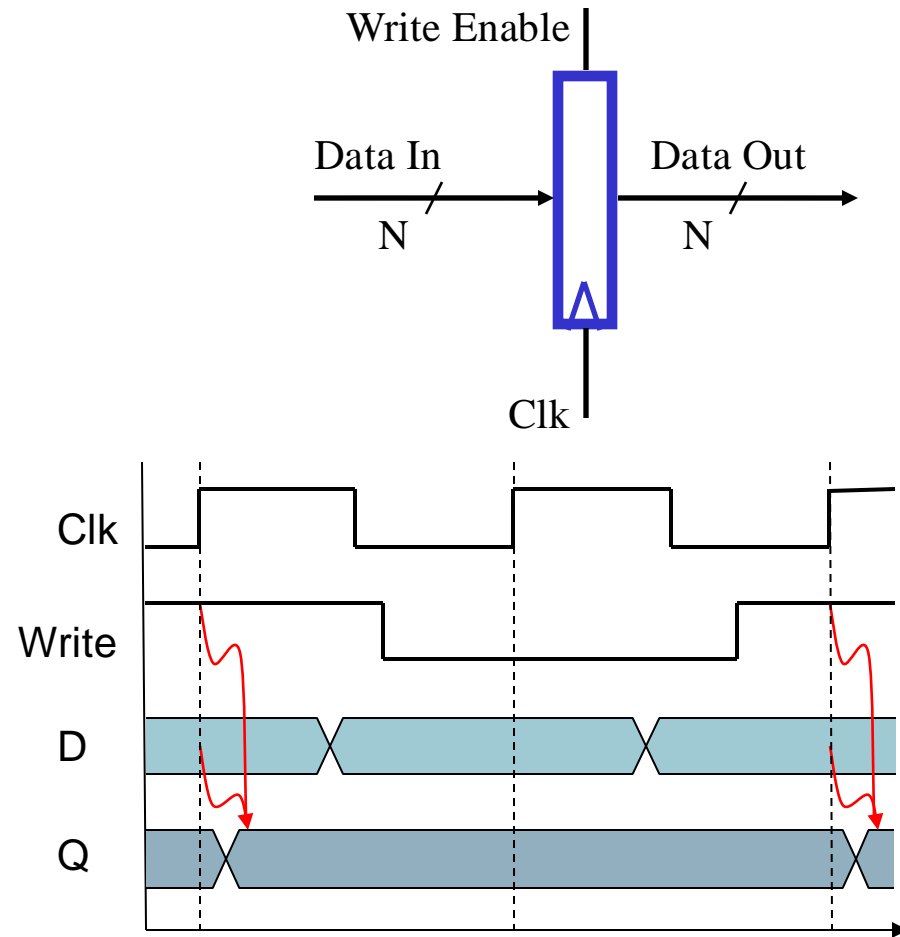
# Storage Element: The Register

- Register
  - Similar to the D Flip Flop except
    - N-bit input and output
    - Write Enable input
- Write Enable:
  - 0: Data Out will not change
  - 1: Data Out will become Data In (on the clock edge)
    - Only updates on clock edge when write control input is 1
    - Used when stored value is required later



 
# Storage Element: Register File

- Register File consists of (32) registers:
  - Two 32-bit output buses
  - One 32-bit input bus
- Register is selected by:
  - **RR1** selects the register to put on bus “Read Data 1”
  - **RR2** selects the register to put on bus “Read Data 2”
  - **WR** selects the register to be written
    - via WriteData when RegWrite is 1
- Clock input (CLK)



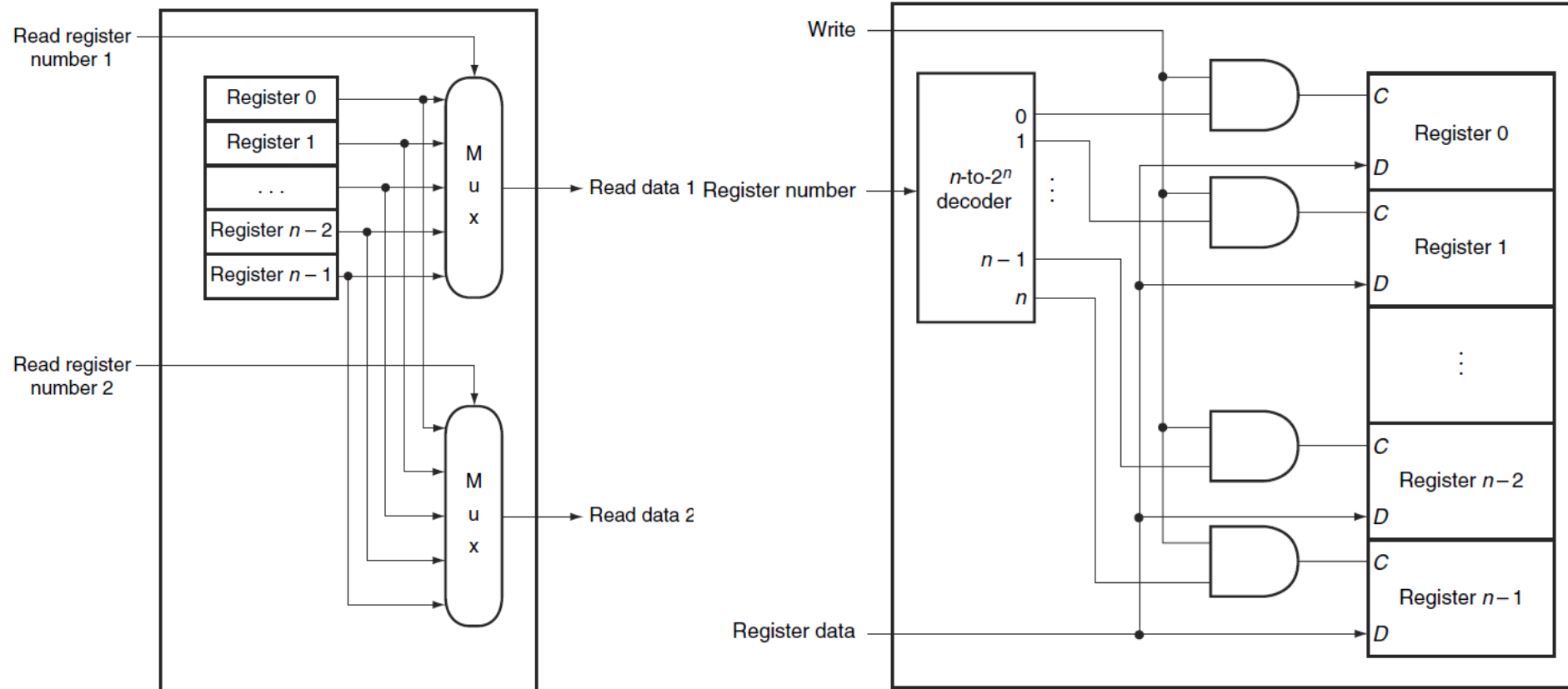
# Inside the Register File

- The implementation of two read ports register file
  - $n$  registers
  - done with a pair of  $n$ -to-1 multiplexors, each 32 bits wide.


 
# Storage Element: Memory

- Memory
  - Two input buses: **WriteData, Address**
  - One output bus: **ReadData**
- Memory word is selected by:
  - Address selects the word to put on ReadData bus
  - If MemWrite = 1: address selects the memory word to be written via the WriteData bus
- Clock input (CLK)
  - The CLK input is a factor ONLY during write operation
  - During read operation, behaves as a combinational logic block:
    - Address valid => ReadData valid after “access time.”



# RTL: Register Transfer Language

- Describes the movement and manipulation of data between storage elements:
  - $R[i]$ 表示寄存器堆中寄存器*i*的内容
  - $M[addr]$ 表示存储单元*addr*的内容
  - 传送方向用 $\leftarrow$ 表示，传送源在右目的在左
  - 程序计数器PC直接用PC表示其内容

$R[3] \leftarrow R[5] + R[7]$

$PC \leftarrow PC + 4 + R[5]$

$R[rd] \leftarrow R[rs] + R[rt]$

$R[rt] \leftarrow Mem[R[rs] + immed]$